

# Logarithmic 16 bit adder using Brent Kung architecture

**Self Project** 

BY

P.Nagasai Goud 203070094

## DEPARTMENT OF ELECTRICAL ENGINEERING

**IIT BOMBAY** 

Main Gate Rd, IIT Area, Powai, Mumbai, Maharashtra 400076

#### Tree Adders

- Tree adders use the idea of carry look ahead addition.
- However, these do not try to implement the complex logic expressions which result from looking ahead all the way.
- Instead, these build up the logic in a tree like structure, where each node performs simple logic operations on the results of the previous node.
- Because of the tree structure used in this, the delay is of the O(logn) for an n bit adder.

For Carry Look Ahead, we had defined


$$K = \overline{A}.\overline{B}$$
,  $G = A.B$  and  $P = A \oplus B$ 

P, G and K can be computed without waiting for Cin.

when K = 1  $C_{out} = 0$  irrespective of  $C_{in}$ .

when G = 1  $C_{out} = 1$  irrespective of  $C_{in}$ .

 when P = 1  $C_{out} = C_{in} \implies$  This is the only case when we must wait for  $C_{in}$  in order to compute  $C_{out}$ 



The least significant bit is indexed as 0 and the most significant bit as n-1

i'th bit accepts  $C_i$  as input carry and produces  $C_{i+1}$  as output carry. Output of the i'th stage is:

$$C_{i+1} = G_i + P_i \cdot C_i \tag{1}$$

 $C_i$  itself is the output of cell no. (i-1). Hence,

$$C_{i+1} = G_i + P_i \cdot (G_{i-1} + P_{i-1} \cdot C_{i-1}) \implies (G_i + P_i \cdot G_{i-1}) + (P_i \cdot P_{i-1}) \cdot C_{i-1}$$

$$C_{i+1} = G_{i,i-1}^2 + P_{i,i-1}^2 \cdot C_{i-1}$$
 (2)


which evaluates  $C_{i+1}$  directly from  $C_{i-1}$ .

- Once the highest order P and G values have been generated, the final carry can be computed in one step from the input carry.
- In principle, we do not need the internal carries at each bit for the final result.
- However, addition is not complete unless all the sum bits have also been generated.

The sum bits are given by:  $S_i = A_i \oplus B_i \oplus C_i = P_i \oplus C_i$ 
 
# **Brent Kung Adder**

- The Brent Kung tree adder is a logarithmic adder of low complexity.
- Values of P and G are computed in a tree fashion
- The figure below shows the generation of P and G values for an 16 bit adder.



we first calculate  $P_i^1, G_i^1$ , with  $i = 0 \dots 15$ 

$$G_i^1 = A_i.B_i, P_i^1 = A_i \oplus B_i$$

Next, using these values, we can generate  $P_{2i+1,2i}^2$ ,  $G_{2i+1,2i}^2$ , with i=0...7

$$G_{2i+1,2i}^2 = G_{2i+1}^1 + P_{2i+1}^1.G_{2i}^1$$
,  $P_{2i+1,2i}^2 = P_{2i+1}^1.P_{2i}^1$ 

Similarly we can find all other higher order G,P values.

After finding all orders of G,P then we can find the carry from equation (1),(2)


With all carry values generated, the corresponding sum values can be calculated using the relation  $Sum_i = P_i^1 \oplus C_i$ 


a	b277	01e7	2573	1d22	0000	2230	ffff	0002	0a08	0c8e	3104	6386	0dc6	0000	0019
		_													
b	2109	0359	0039	0000	003a	2109	0001	0039	19b8	1674	7f4b	3b8d	04d3	0000	007d
Cin	1														
	1004	V 0544		4 100									1000		V 0007
Sum	d381	0541	25ac	1d23	003a	433a	0000	003b	23c1	2303	b050	9f14	1299	0001	0097
Cout													19		
Cour															

```
0 << Starting the Simulation >>
                        0 A = 45687, B = 8457, Cin= 1 : Sum = 54145, Cout = 0
time=
                                487, B = 857, Cin= 1 : Sum = 1345, Cout = 0
time=
                       40 A = 9587, B =
                                            57, Cin= 0 : Sum = 9644, Cout = 0
time=
                       60 A = 7458, B =
                                             0, Cin= 1 : Sum = 7459, Cout = 0
time=
                       80 A =
                                  0, B =
                                            58, Cin= 0 : Sum =
                                                                  58, Cout = 0
time=
                      100 A = 8752, B = 8457, Cin= 1 : Sum = 17210, Cout = 0
time=
                      120 A = 65535, B =
                                             1, Cin= 0 : Sum =
                                                                   0, Cout = 1
time=
                      140 A =
                                  2, B =
                                            57, Cin= 0 : Sum =
                                                                  59, Cout = 0
time=
                      160 A = 2568, B = 6584, Cin= 1 : Sum = 9153, Cout = 0
time=
                      180 A = 3214, B = 5748, Cin= 1 : Sum = 8963, Cout = 0
time=
                      200 A = 12548, B = 32587, Cin= 1 : Sum = 45136, Cout = 0
time=
                      220 A = 25478, B = 15245, Cin= 1 : Sum = 40724, Cout = 0
time=
                      240 A = 3526, B = 1235, Cin= 0 : Sum = 4761, Cout = 0
time=
                      260 A =
                                  0, B =
                                             0, Cin= 1 : Sum =
                                                                   1, Cout = 0
time=
                                 25, B =
                                          125, Cin= 1 : Sum =
                                                                 151, Cout = 0
time=
                      280 A =
time=
                                852, B =
                                             8, Cin= 1 : Sum =
                                                                 861, Cout = 0
```

Figure 1: Adder output for Appropriate test vectors

	Logic Delay	Route Delay	Total Delay
Brent Kung	11.268ns	9.505ns	20.773ns
RCA	13.288ns	15.453ns	28.741ns

 

 

These delays are calculated in Xilinx Software.

Family :- Spartan-3 Device :- XC3s200

Package:-FT256 Speed: -5

## Reference

• EE 671 Lectures IIT-Bombay by Prof.K.Dinesh Sharma